

CND 221: Advanced Full Custom VLSI Design

Assignment #: 02

Section #: 21


Submitted by:

Student Name	ID
Eslam Asaad Mahmoud	V23010461


Submitted to TA: Mohamed Nabil

1. C2MOS latch

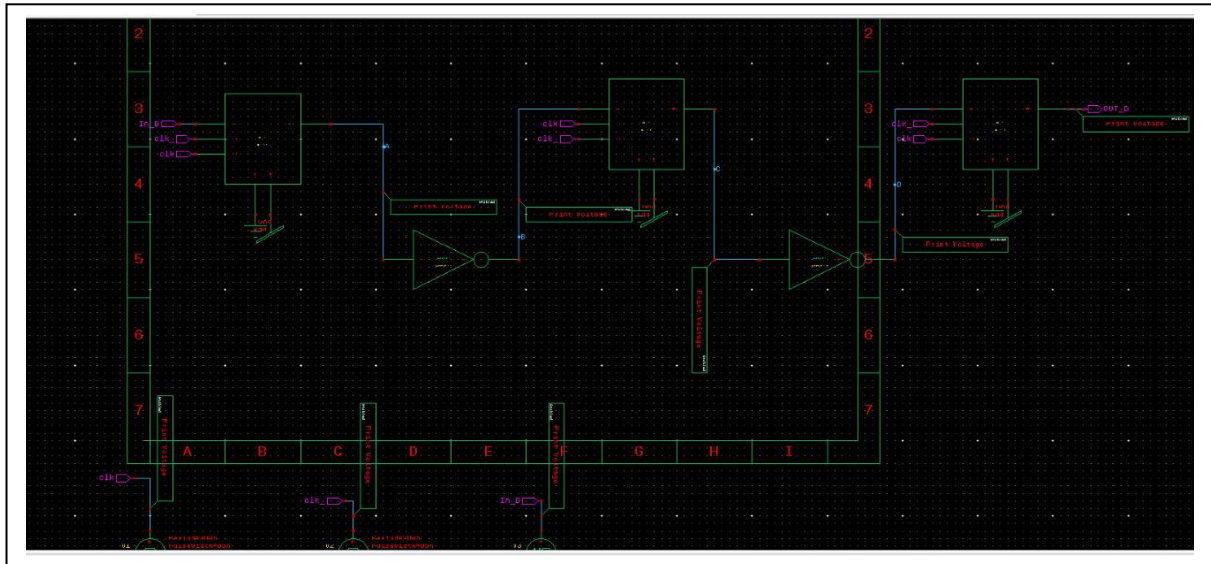i. Add screenshot from your **schematic**:



ii. Waveform

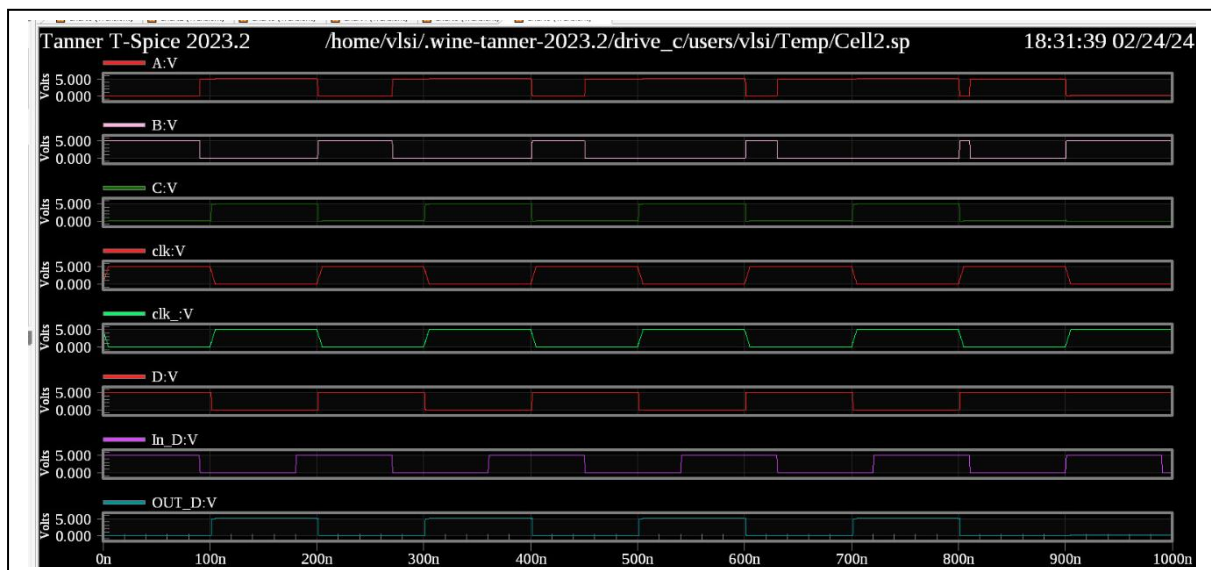

iii. Layout: clean DRC and LVS

